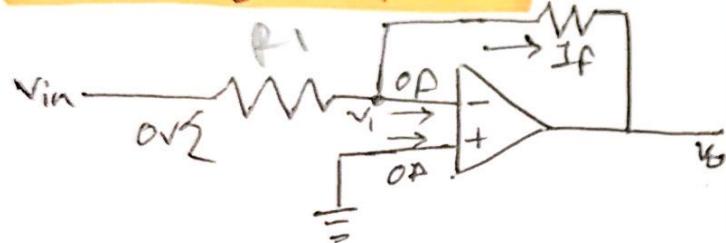


Inverting Amplifier RF




$$V_0 = \left(-\frac{R_F}{R_1} \right) \times V_{in}$$

$$A = \left(-\frac{R_F}{R_1} \right)$$

$$V_I = 0$$

$$\frac{V_1 - V_{in}}{R_1} + \frac{V_1 - V_0}{R_F} + OA = 0$$



Non-Inverting Amplifier

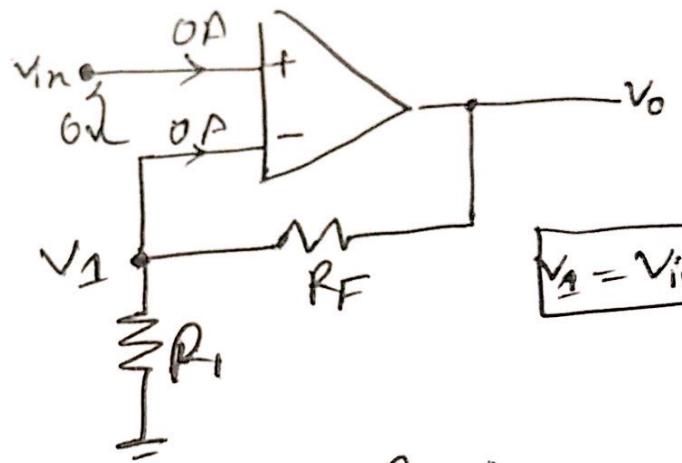

$$V_0 = V_{in} \left(1 + \frac{R_F}{R_1} \right)$$

$$A = \left(1 + \frac{R_F}{R_1} \right)$$


Open Loop

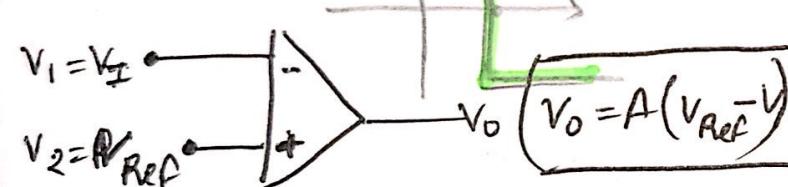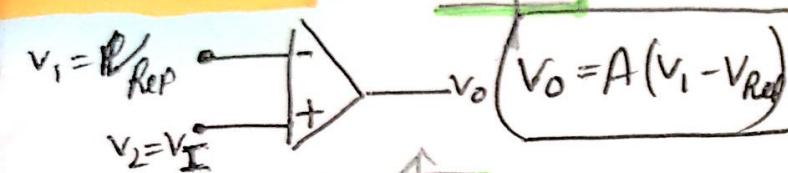


comparators

$$V_d > 0 \Rightarrow V_a > V_b \Rightarrow (V_s+) \Rightarrow V_o = A \cdot 10$$
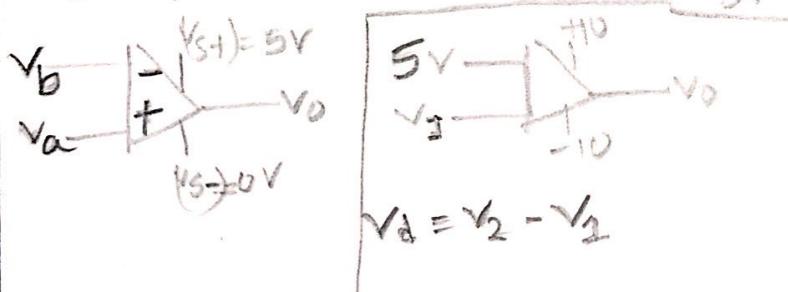
$$V_d < 0 \Rightarrow V_a < V_b \Rightarrow (V_s-) \Rightarrow V_o = A \cdot 0$$



Negative Feedback

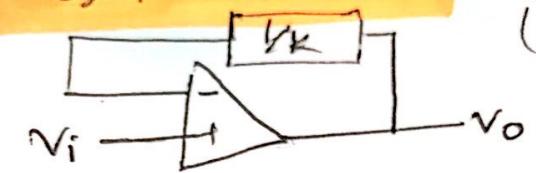


$K = 10 \Leftrightarrow 10$
 $(1/10) + n$ of
 output is
 feedback
 to (+) input

$$v_o = Av_i \quad v_o = Kv_i \quad A = 3 \quad v_i = 5V \quad k = 10$$

$$v_o = 0V \quad v_o = 15 \\ v_- = \frac{v_o}{10} = 0 \quad v_- = \frac{15}{10} = 1.5V \\ v_d = v_+ = v_o = 5 - 0 \\ v_d = v_+ - v_- = 5 - 1.5 \\ v_d = 3.5$$

$$v_o = Av_d \\ = 3 \times 3 \\ = 9 \\ v_o = Av_d \\ = 3.5 \times 3 \\ = 10.5$$

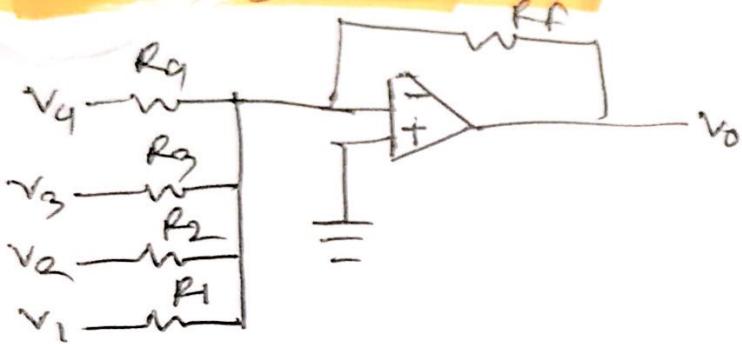
$$v_o = 10.5 \\ v_- = \frac{10.5}{10} = 1.05 \\ v_d = v_+ - v_- = 5 - 1.05 \\ v_d = 3.95 \\ v_o = Av_d \\ = 3 \times 3.95 \\ = 11.85$$



$$v_0 = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3 - \frac{R_f}{R_4} v_4$$

~~300Ω totat~~


Buffer

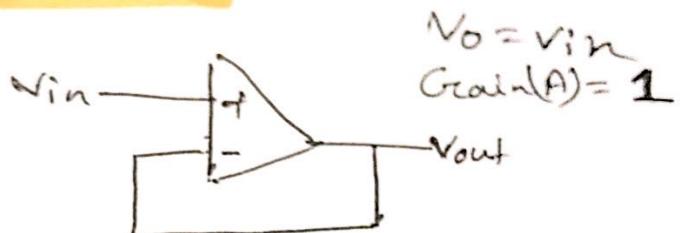

$+$ $-$ $300\Omega \text{ totat}$ (3) on

$+$ $-$ $300\Omega \Delta \Delta$ (6) off

Differentiator

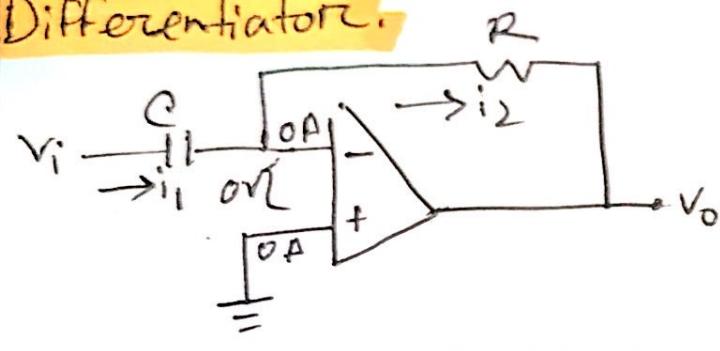


$$C \cdot i_1 = C \cdot \frac{dV_0}{dt} = C \cdot \frac{d(V_i - 0)}{dt} = C \frac{dV_i}{dt}$$

$$R \cdot i_2 = \left(\frac{0 - V_0}{R} \right) = -\frac{V_0}{R}$$

$$i_1 = i_2$$

$$V_0 = -RC \cdot \frac{dV_i}{dt}$$

Integrator

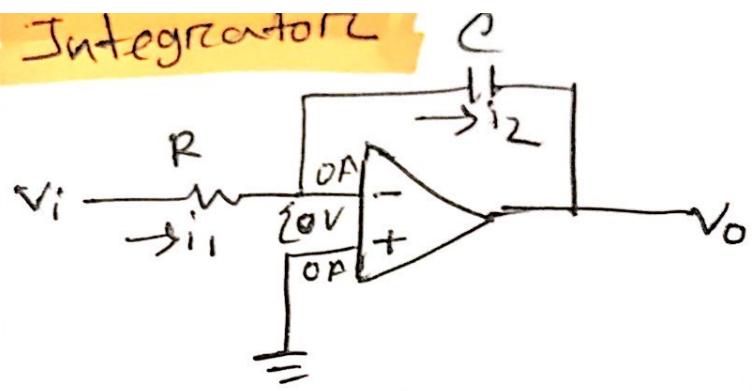


$$R \cdot i_1 = \left(\frac{V_i - 0}{R} \right) = \frac{V_i}{R}$$

$$R \cdot i_2 = C \cdot \frac{dV_0}{dt} = C \frac{d(0 - V_0)}{dt} = -C \frac{dV_0}{dt}$$

$$i_1 = i_2 \quad \frac{dV_0}{dt} = -\frac{V_i}{RC}$$

$$\Rightarrow V_0 = -\frac{1}{RC} \int V_i dt$$

Op-Amp

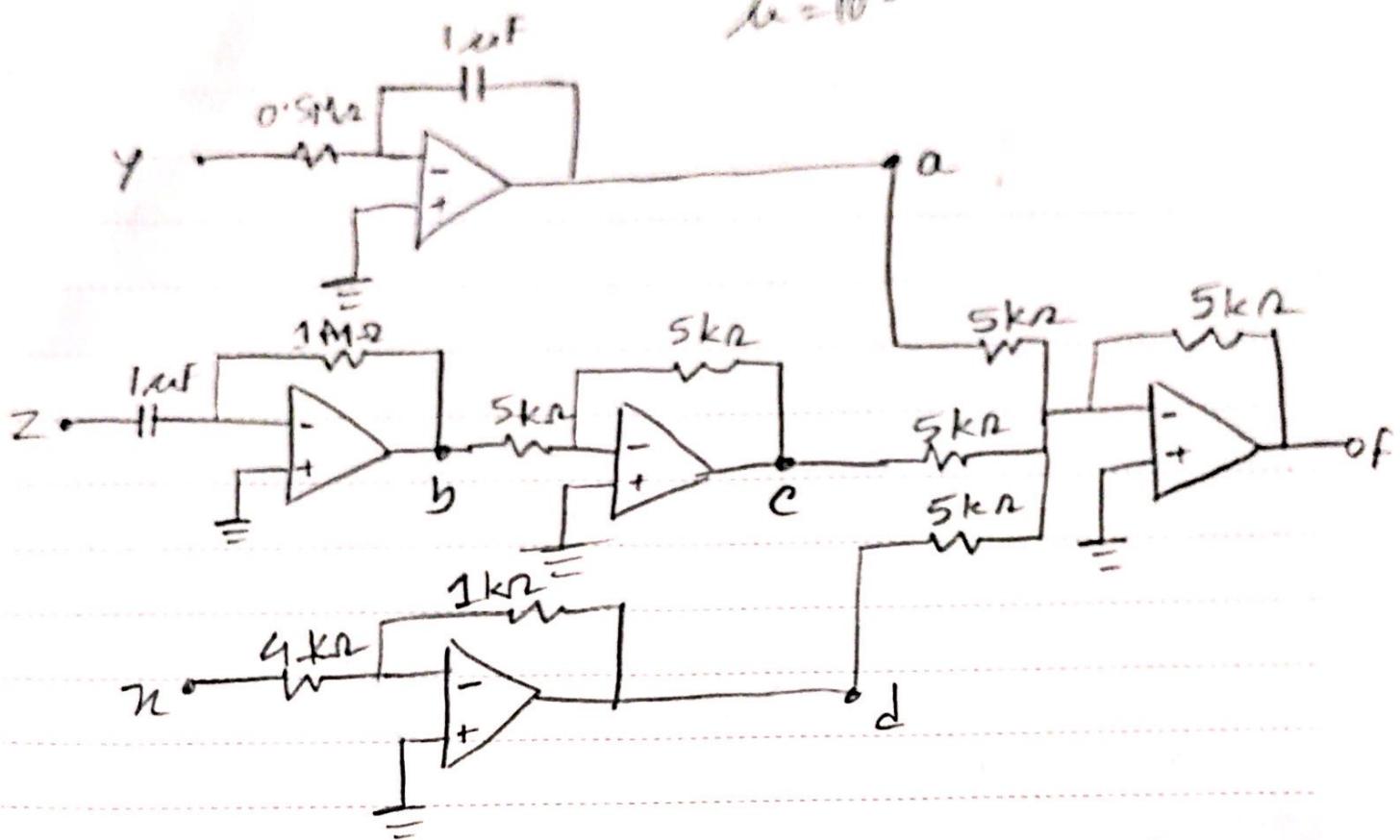

$$a = -\frac{1}{RC} \int v_d dt = -\frac{1}{0.5 \times 1} \int y dt = -2 \int y dt$$

$$b = -RC \cdot \frac{dv_i}{dt} = -1 \cdot \frac{dz}{dt} = -\frac{dz}{dt}$$

$$c = \left(-\frac{5}{5}\right) \times \left(-\frac{dz}{dt}\right) = -\frac{dz}{dt}$$

$$d = -\frac{1}{4} n = -\frac{n}{4} = -0.25n$$

$$f = -\frac{R_f}{R_1} v_1 + \frac{R_f}{R_1} v_L - \frac{R_f}{R_1} v_3$$


Goodbac-3S

$$= -v_1 - v_2 - v_3$$

$$= (-2 \int y dt) - \left(\frac{dz}{dt}\right) - (-0.25n)$$



Fibosyl

$R_f = R_1$
$S = 5$

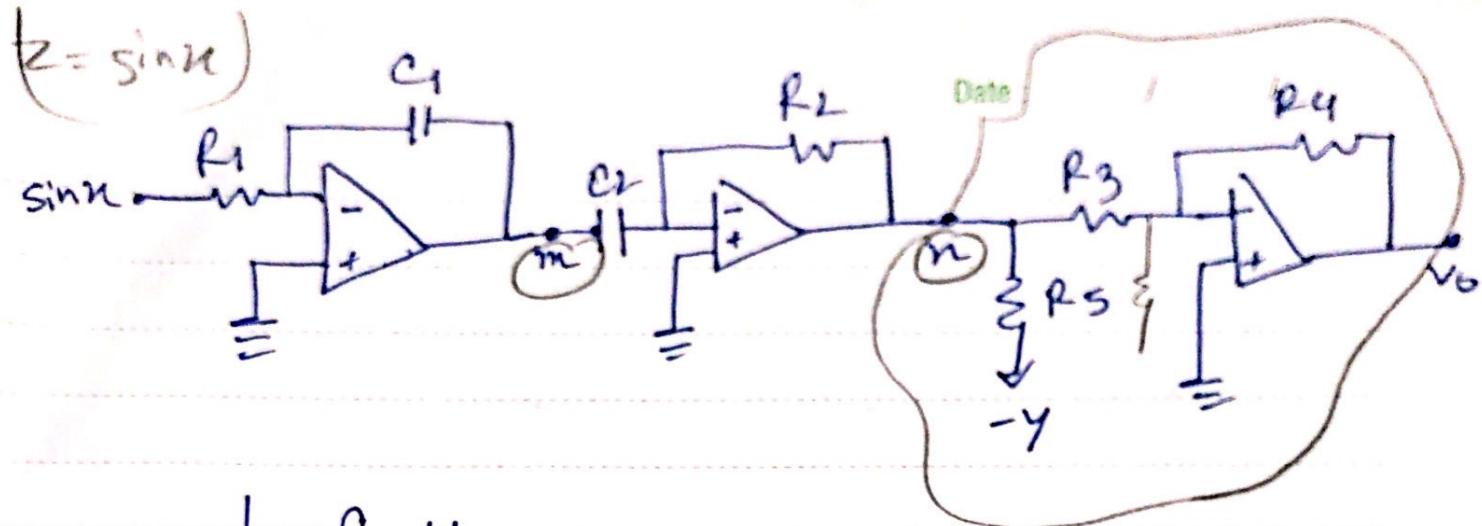

$$m = -\frac{1}{R_1 C_1} \int z dt$$
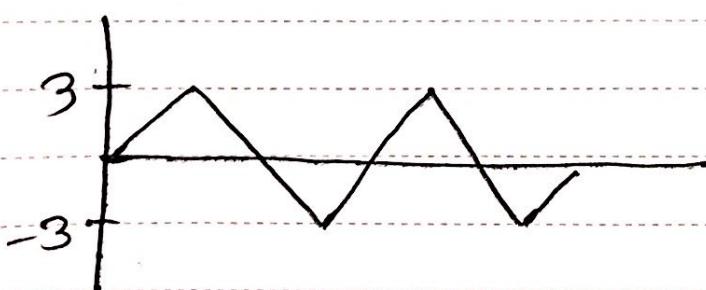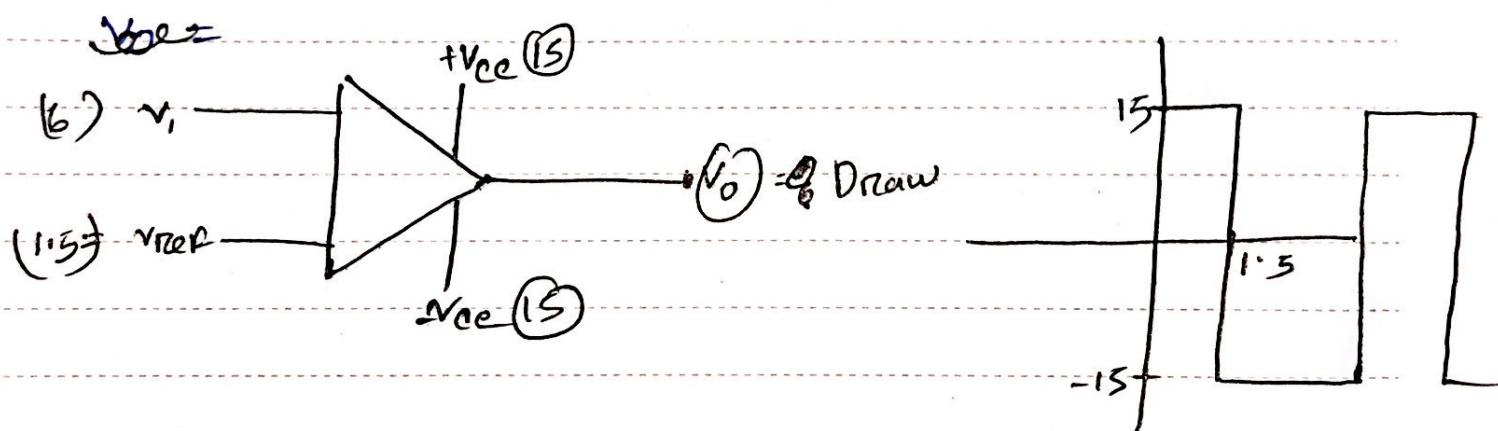
$$\begin{aligned} n &= -R_2 C_2 \frac{dm}{dt} = -R_2 C_2 \cdot \frac{d}{dt} \left(-\frac{1}{R_1 C_1} \int z dt \right) \\ &= \frac{R_2 C_2}{R_1 C_1} \cdot (z) \end{aligned}$$



$$v_o = \left(-\frac{6}{3}\right) v_a = -2 v_a$$

$$v_o = (-2 \times 3) = -6 V$$


$$v_o = (-3 \times -2) = 6 V$$

Goodbac-3S

Gibosyl

I-V

Date

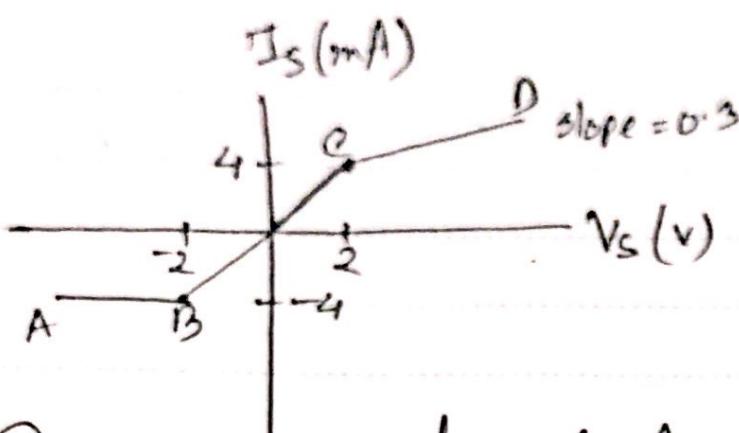

$$mA = 10^3$$

(a) AB = current = $-4mA$

$$BC = \text{Resistor} = \frac{1}{m} = \frac{1}{y-y_1}{n-n_1} = \frac{1(n-n_1)}{y-y_1} = \frac{2-(-2)}{4-(-4)} \times 10^3 = 500\Omega$$

$$CD = (y = mx + c)$$

point (2, 4)

$$m = 0.3$$

$$R = \frac{1}{m} = \frac{1}{0.3} = 3.33\Omega$$

$$\therefore 4 \times 10^3 = 0.3 \times 2 + c$$

$$\Rightarrow c = 0.596$$

$$\frac{-V_o}{R} = 0$$

$$\Rightarrow V_o = -1.98V$$

(b) $V_S = 3V$


$$CD = y = mx + c$$

$$\Rightarrow I_S = mV_S + c$$

$$\Rightarrow I_S = 0.3 \times 3 + 0.596 = 1.496A$$

Diode

Diode logic

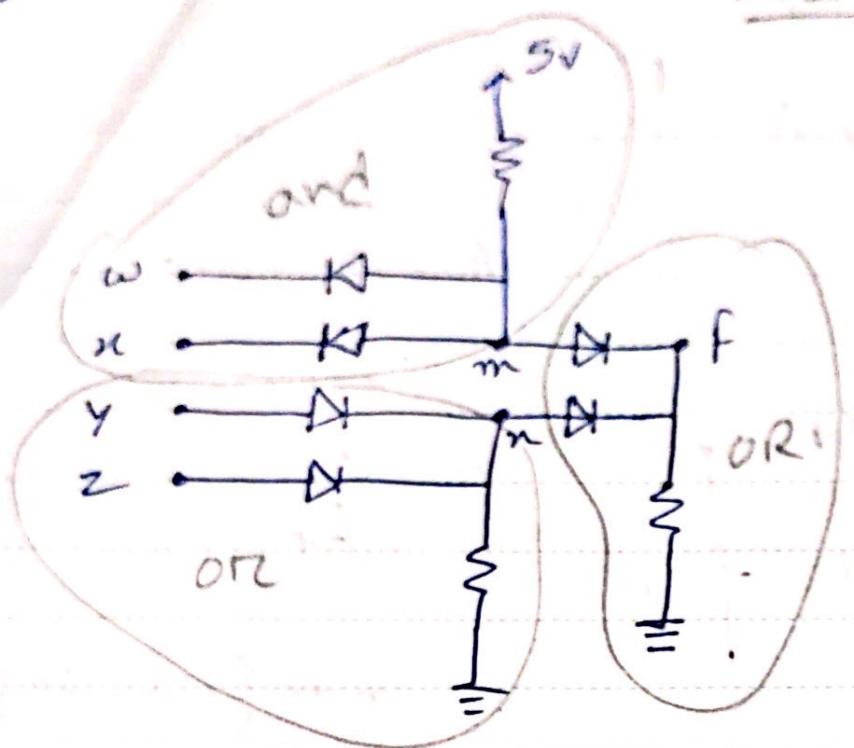

$$\text{AND} = (+5V)$$

$$\text{OR} = \text{GND}(0V)$$

④ $f = m + n$
 $= w \bar{x} + (y + z)$

⑤ $w = -x = 2y = 3z = 5$ determine f ~~Req~~ (c.v.d
 and ideal) ($V_d = 0.7V$)

$$\text{AND} = \min \{\text{inputs}\}$$

$$\text{OR} = \max \{\text{inputs}\}$$

$$w = 5V$$

$$x = -5V$$

$$2y = 5 \Rightarrow y = 5/2 = 2.5V$$

$$3z = 5 \Rightarrow z = 5/3 = 1.67V$$

$$m = \min \{5, -5\} = -5$$


$$n = \max \{2.5, -1.67\} = 2.5$$

$$f = \max \{2.5, -5\} = 2.5$$

for Ideal

Goodbac-3S

Fibosyl

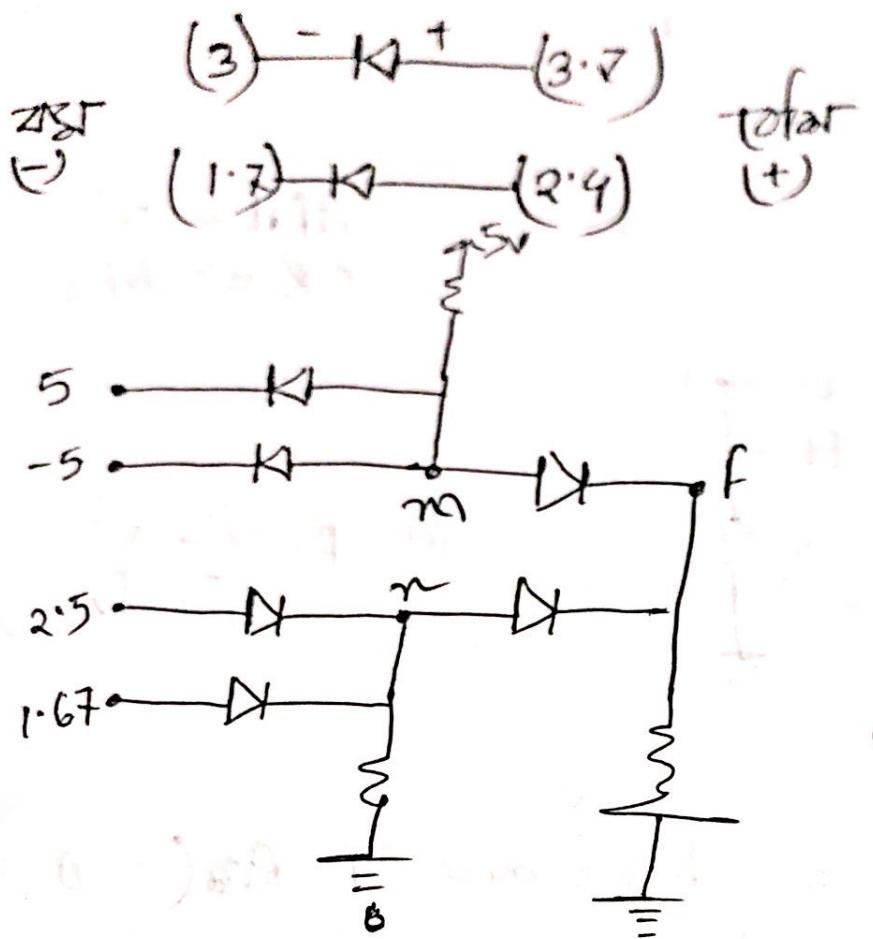

$$And = \min\{5, -5\}$$

$$= -5$$

$$m = (-5 + 0.2) \\ = (4.3)$$

$$OR = \max\{2.5, 1.67\}$$

$$= 2.5$$

$$n = (2.5 - 0.2) \\ = 1.8$$


$$f = \max\{-4.3, 1.8\} - 0.2$$

$$= \cancel{2.5} 1.8 - 0.2$$


$$= 1.1 \text{ V} \quad (\text{CVD model})$$

Diode Assumption

Date _____

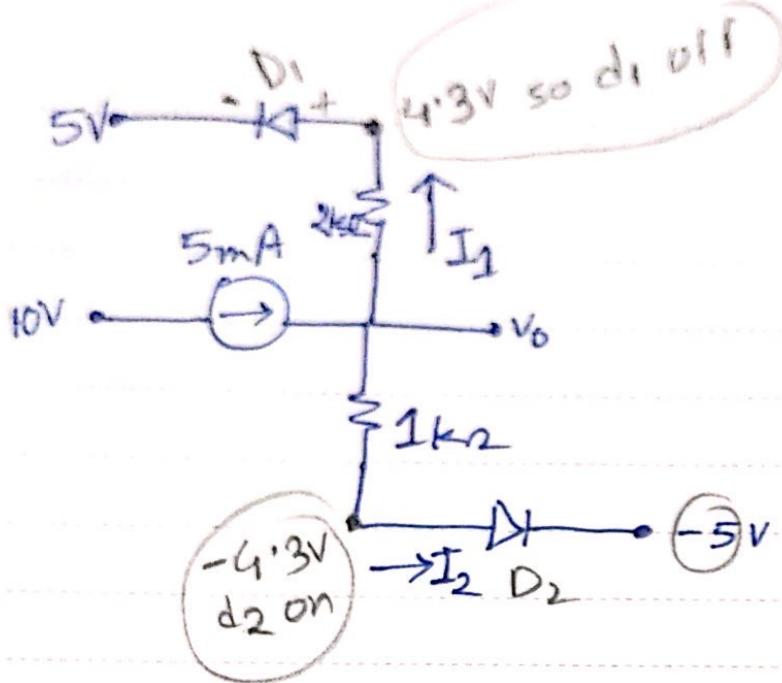


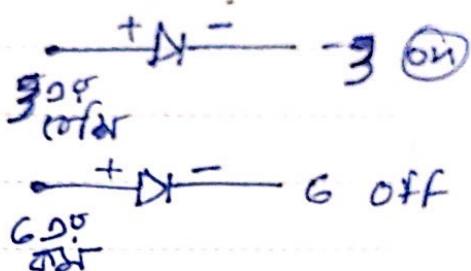Diode 5V possible
total voltage 24VDC
diode on 0.7V enough



D₁ off and D₂ on 2nd

→ D₁ off & I₂ current flow (3.2mA)

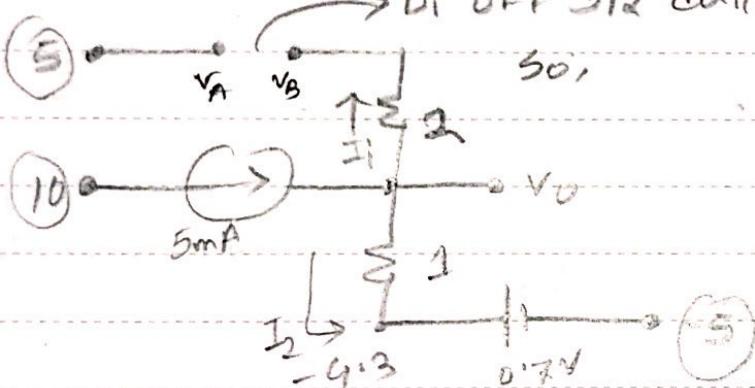

How to test

Diode off → test the voltage across the diode

$$\frac{V_0 - (-4.3)}{1} = 5 \text{ mA}$$

$$\Rightarrow V_0 = 0.7$$

Diode on → test the current across the diode

$$I_2 = \frac{V_0 - (4.3)}{1} = \frac{0.7 + 4.3}{1} = 5 \text{ mA.}$$

Verify

on → current (+)

Veri


$$V_0 - V_B = 5 - 4.3 = 0.7$$

$$V_B = 10 - 0.7 = 9.3$$

OFF → voltage opposite.

Gibosyl

Goodbac-3S

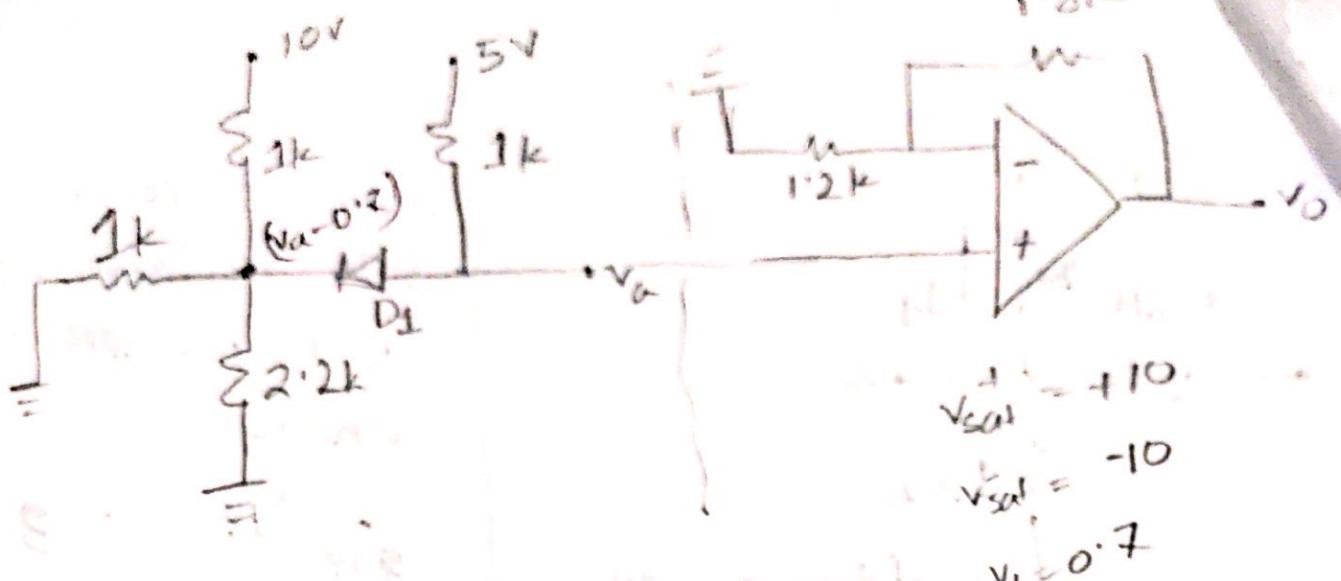

$$v_a = 9.84 \text{ V}$$

$$(v_a - 0.7)(1 + 1 + \frac{1}{2.2}) + v_a - 10 - 5 = 0$$

$$\Rightarrow v_a = 9.84$$

$$I_{D1} = 0.16 \text{ mA} = \left(\frac{5 - v_a}{1} \right)$$

$I_{D1} > 0$ no current flows into op-amp terminals.
So, assumption is true.

Non-inverting,

$$v_o = \left(1 + \frac{R_F}{R_1} \right) v_a$$

$$= \left(1 + \frac{1.8}{1.2} \right) 9.84$$

$$= 12.1 \text{ V}$$

$$v_o > v_{sat}^+$$


$$\text{So, } v_o = v_o = (+10)$$

$$\text{and } (v_d = 0.7 / 0.5 \text{ V})$$

$$\text{ideal } (v_d = 0 \text{ V})$$

Diode

Date:

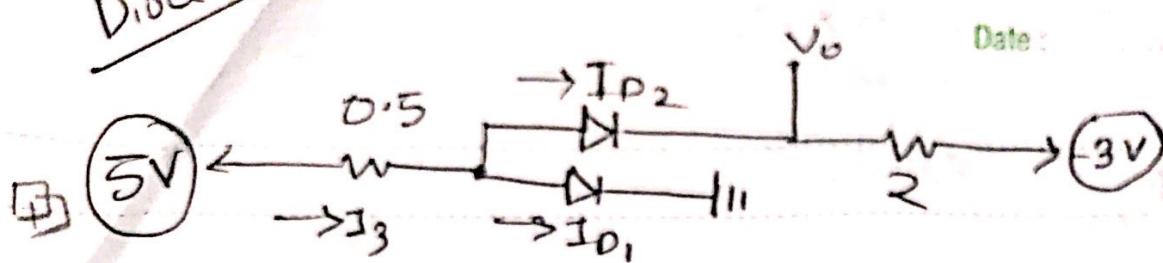


$$V_d = 0.6 \text{ V}$$


$$\begin{aligned} I_3 &= I_{D1} + I_{D2} & \frac{5 - V_a}{0.5} &= I_3 & \frac{V_o + 3}{2} &= I_{D2} \\ V_a - 0 &= 0.6 & \Rightarrow I_3 &= 8.8 \text{ A} & \Rightarrow I_{D2} &= 1.5 \text{ A} \\ \Rightarrow V_a &= 0.6 \end{aligned}$$

$$\begin{aligned} \therefore I_{D1} &= 7.3 \text{ A} & V_o - V_a &= 0.6 \\ & & \Rightarrow V_o &= 0 \end{aligned}$$

Assumption correct
D₁ and D₂ on.

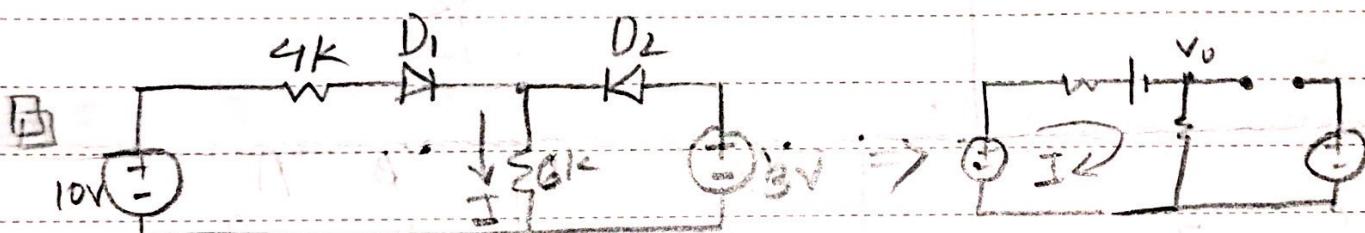

D₁ = ON and D₂ = ON

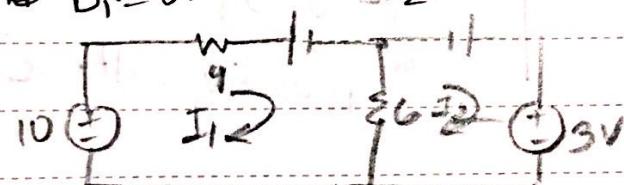

$$-10 + 4I_1 + 0.7 + 6(I_1 - I_2) = 0$$

$$\Rightarrow 10I_1 - 6I_2 = 9.3 \quad \textcircled{1}$$

$$6(I_2 - I_1) - 0.7 + 3 = 0$$

$$\Rightarrow 6I_2 - 6I_1 = -2.3$$

$$\Rightarrow 6I_1 - 6I_2 = 2.3 \quad \textcircled{11}$$

$$I_1 = 1.75, I_2 = 1.36$$

D₁ = ON, D₂ = OFF

$$I(4+6) - 10 + 0.7 = 0$$

$$\Rightarrow I = 0.93 \text{ mA}$$

$$I_{d1} > 0$$

$$V_o = 6 \times 0.93 = 5.58$$

$$\begin{aligned} V_{d2} &= 3 - 5.58 \\ &= -2.58 \leq 0.7 \end{aligned}$$


Assumption right.

Goodbac-3S

$I_{d2} = -1.36$ assumption wrong

fibosyl

$$B) V_0 = 0.8V$$

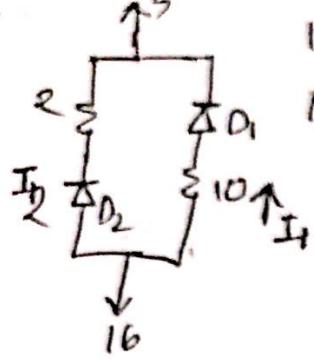

$$10 - 5 = 2I_2 + 0.8 + I_3$$


$$10 - 5 = 10I_1 + 0.8 + I_3$$

$$I_3 = I_2 + I_1$$

$$I_1 = 0.6375 > 0$$

$$I_2 = 3.1875 > 0$$

$$I_3 = 3.825$$

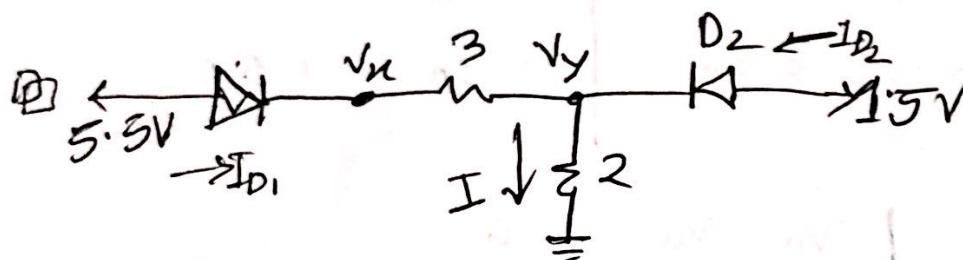

$$V_x = (5.5 - 0.5) = 5V$$

$$I_{D2} = 0$$

$$I_{D1} = I$$

$$\frac{V_x - 0}{2+3} = I$$

$$\Rightarrow I = \frac{5}{5} = 1mA = I_{D1}$$

$$\therefore I_{D1} > 0$$

current positive


$$\frac{V_y - 0}{2} = 1$$

$$\Rightarrow V_y = 2$$


$$\begin{aligned} V_B - V_A \\ = 1.5 - 2 \\ = (-0.5) \end{aligned}$$

opposite voltage

so assumption is correct.


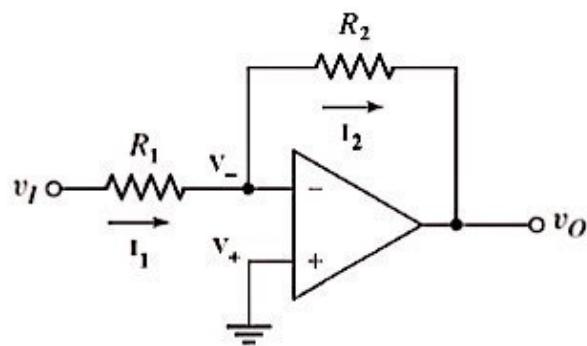


- Design an inverting amplifier (i.e., find the values of R_1 and R_2 of the circuit shown in the Figure above) in such a way that the voltage gain is -5 .
- Consider the circuit you drew in (a) again. Assume the input $v_i = 0.1 \sin\omega t$ (V) has a maximum current rating of $5 \mu A$. What design changes, if any, are required for this input, if the voltage gain remains the same?
- Draw the input and output waveforms of the circuit you designed in (c).

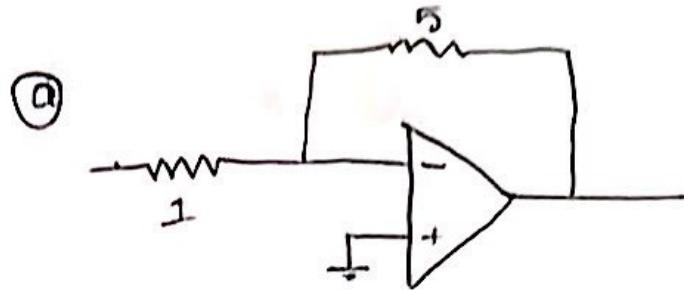




(b)
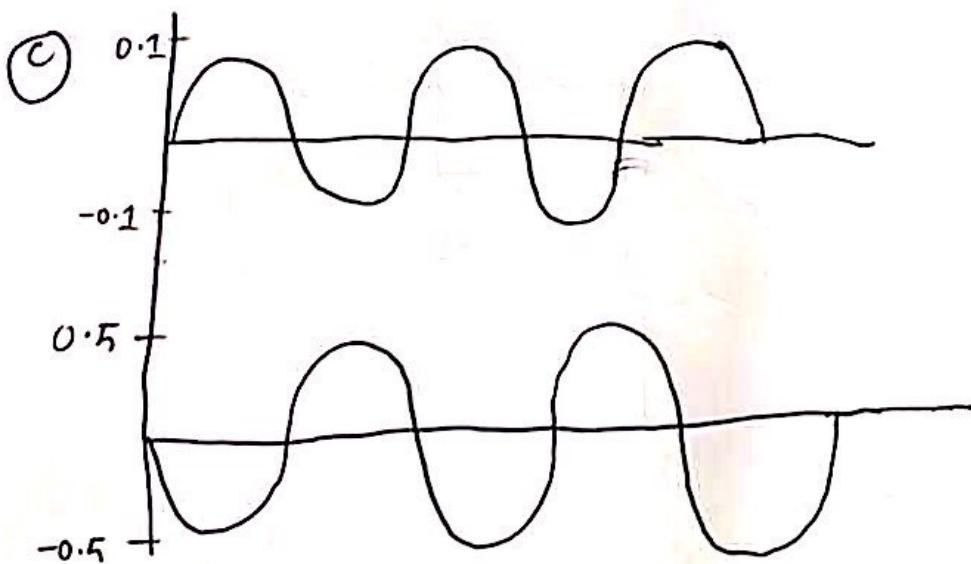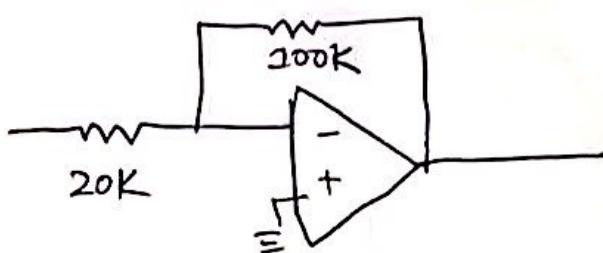
$$R_{in} = \frac{0.1}{5 \times 10^{-6}} = 20K\Omega$$



J class miss disilam sefa.




Method of assumed states:

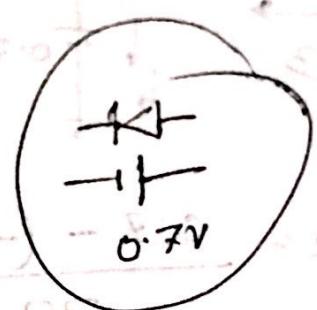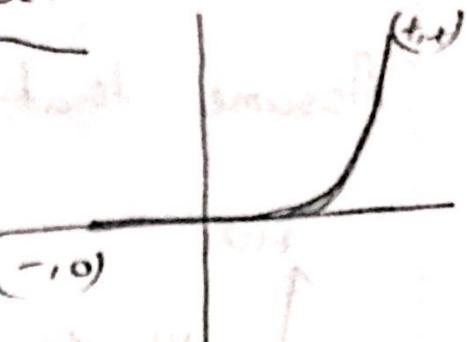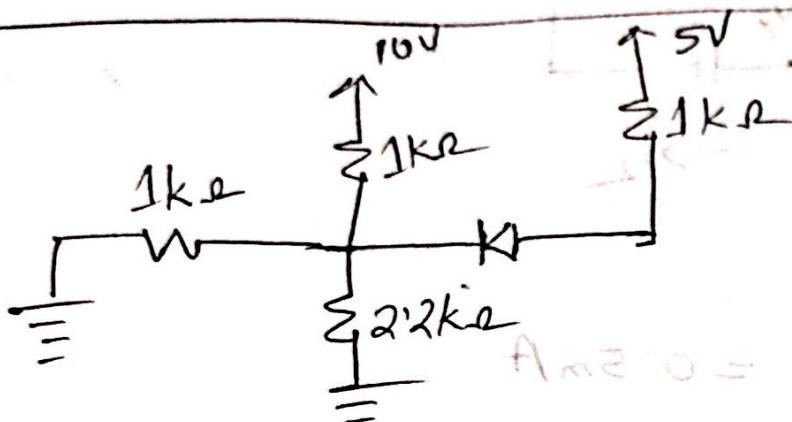

Diode
On → current direction test

Off → voltage polarity test.

Assuming that the diode is active,

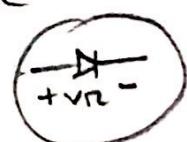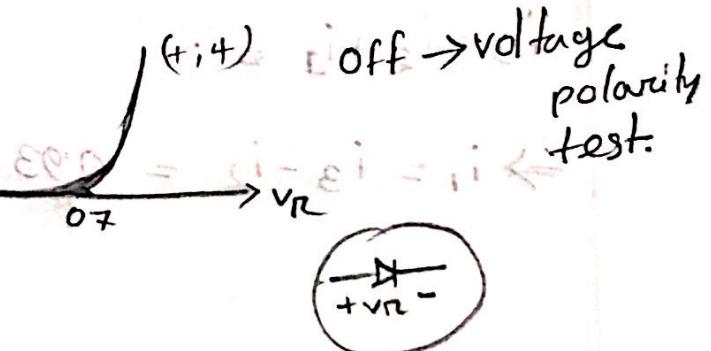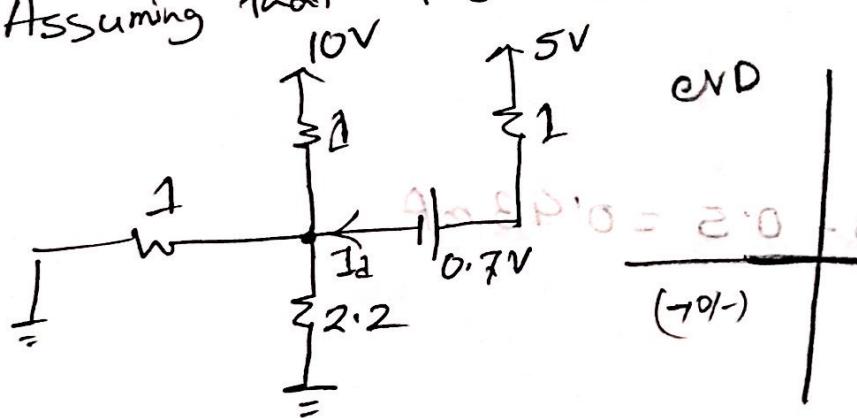


$$\frac{v_1}{2.2} + \frac{v_1 - 10}{1} + \frac{v_1}{1} + \frac{v_1 + 0.7 - 5}{1} = 0$$


$$\Rightarrow v_1 = 4.139$$

$$v_1 = 4.139 + 0.7 = 4.839 \text{ V}$$
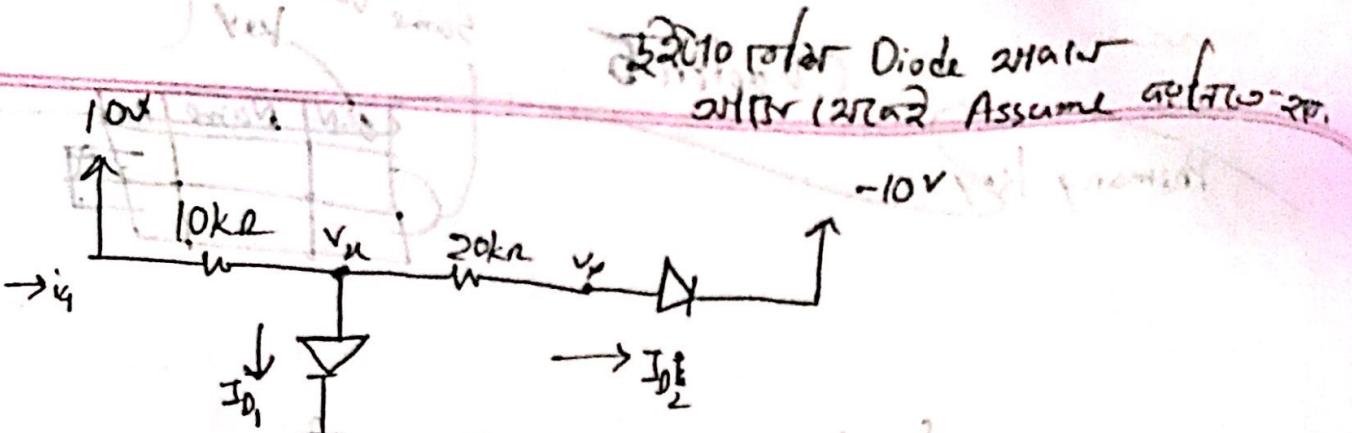
$$i_d = \left(\frac{5 - 4.83}{1} \right) = 0.17 \text{ mA}$$



Assume that D_1 and D_2 both are on,

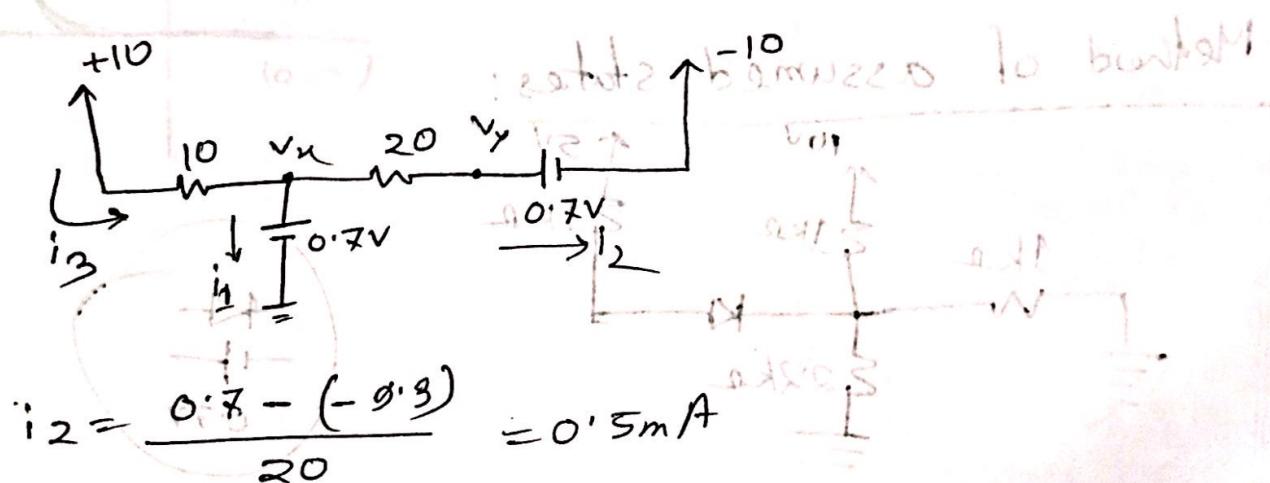

$$i_3 = \frac{10 - 0.7}{10} = 0.93 \text{ mA}$$


about 0.5 mA current

$$i_3 = i_2 + i_1 \approx 0.5 + 0.5 = 1 \text{ mA}$$


$$\Rightarrow i_1 = i_3 - i_2 = 0.93 - 0.5 = 0.43 \text{ mA}$$

$$D = \frac{2.303 + V}{T} + \frac{V}{T} + \frac{2.303}{T}$$


I-V Characteristics.

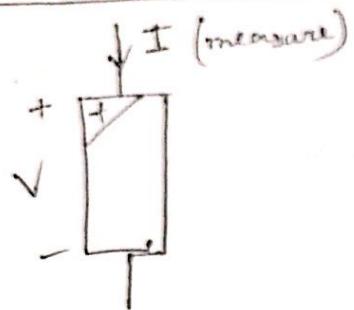

$$V = IR \Rightarrow R = \frac{V}{I}$$


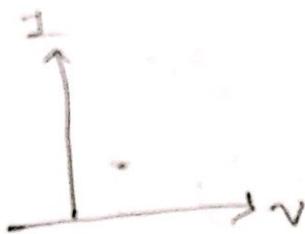

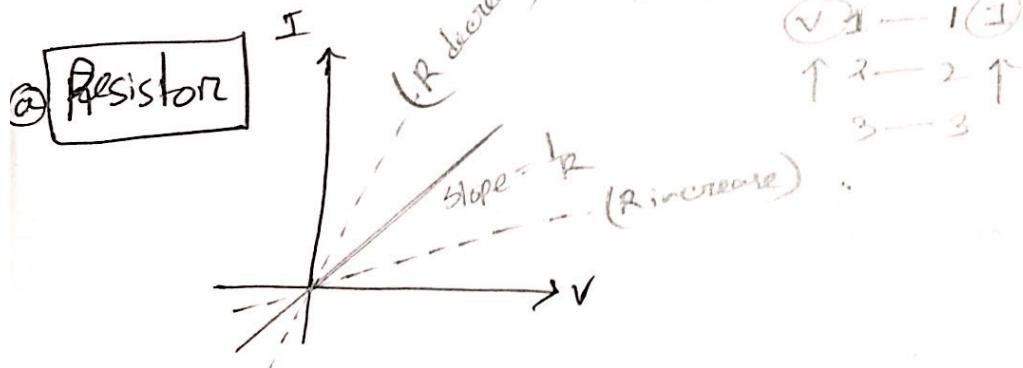
$$I = \frac{V}{R} = \frac{1}{R} \cdot V \quad \boxed{\text{For resistor only}}$$





$$\begin{aligned} I &= \frac{1}{2} V \\ &= \frac{1}{3} V \\ &= \frac{1}{4} V \\ &= \frac{1}{5} V \\ &= \frac{1}{6} V \end{aligned} \quad \begin{array}{l} R = 2 \Omega \\ 2 \Omega \text{ at } 5 \\ \text{slope } 2 \Omega \\ 2 \Omega \text{ at } 6 \\ \text{slope } 3 \Omega \\ 3 \Omega \text{ at } 4 \\ \text{slope } 4 \Omega \\ 4 \Omega \text{ at } 3 \\ \text{slope } 5 \Omega \\ 5 \Omega \text{ at } 2 \\ \text{slope } 6 \Omega \end{array}$$

⑤ **Current Source:**

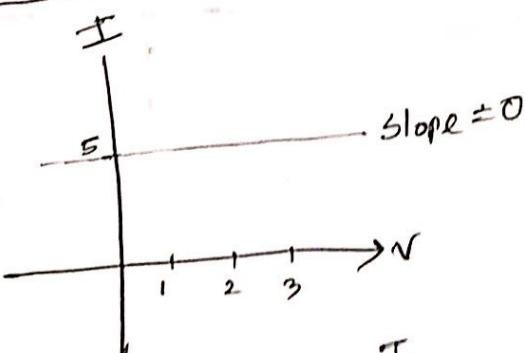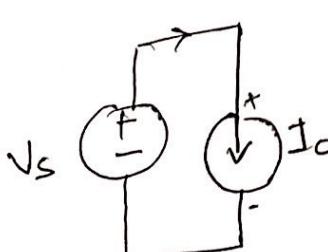




V	I
1V	5A
2V	5A
3V	5A

$(y = 5)$

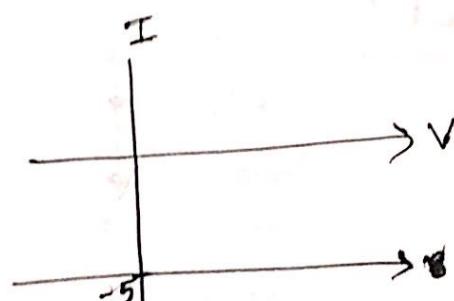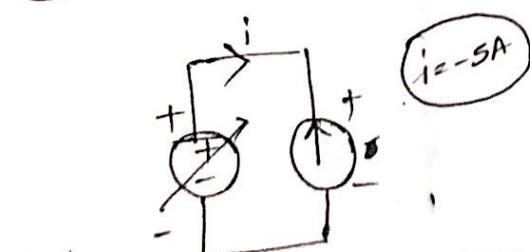


ideal current source $i = -5A$ current may change with voltage but flow direction is constant.

① Voltage source:

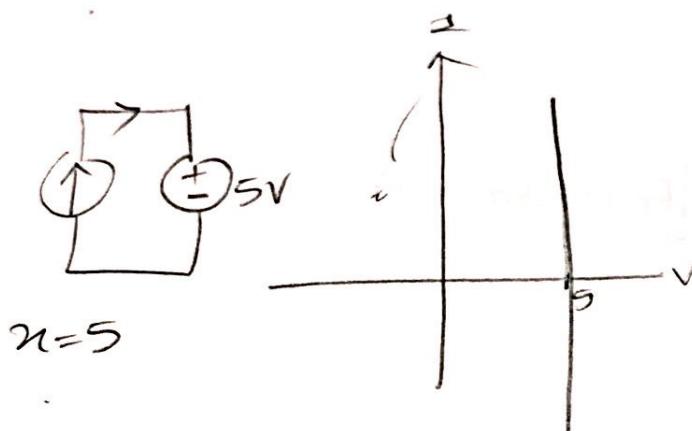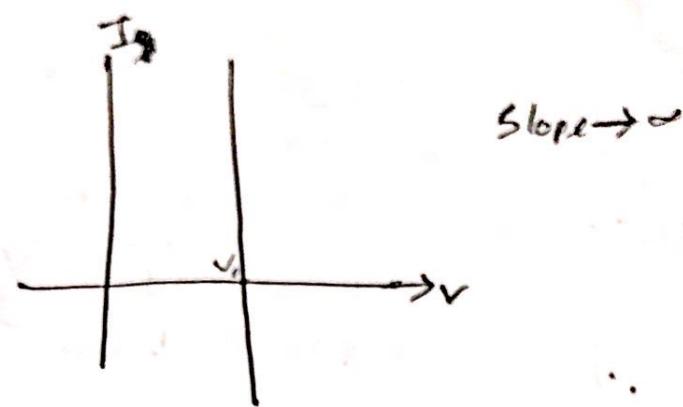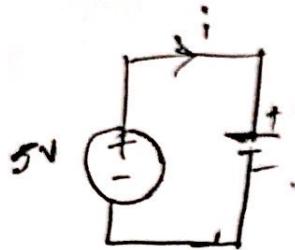


V	I
$5V$	$1A$
$5V$	$2A$
$5V$	$3A$

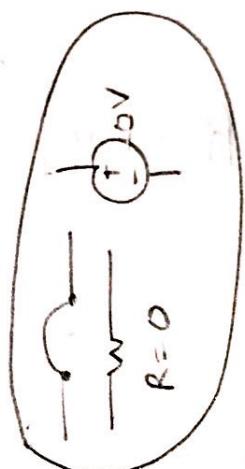


② Degenerate element:

② open circuit:

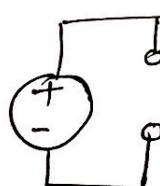


V	I
$5V$	0
$6V$	0
$7V$	0

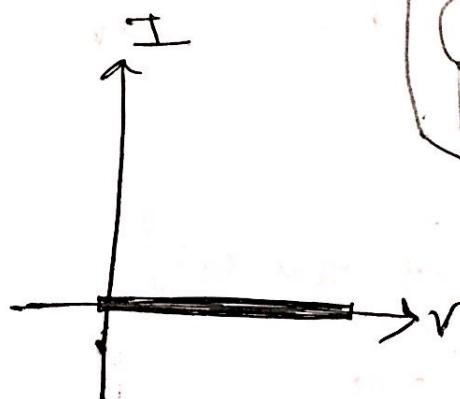

③ short circuit:

V	I
$0V$	$5A$
$0V$	$6A$
$0V$	$7A$

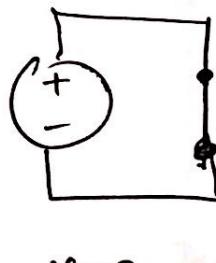

$$x=0$$



Linear element

② Voltage + resistor

$$-V_s + V_o + IR = 0$$



$$\Rightarrow IR = V_s - V_o$$

$$\Rightarrow I = \frac{V_s - V_o}{R}$$


$$= \frac{V_s}{R} - \frac{V_o}{R}$$

$$= \frac{1}{R} \cdot V_s - \frac{V_o}{R}$$

$$Y = mX + c$$

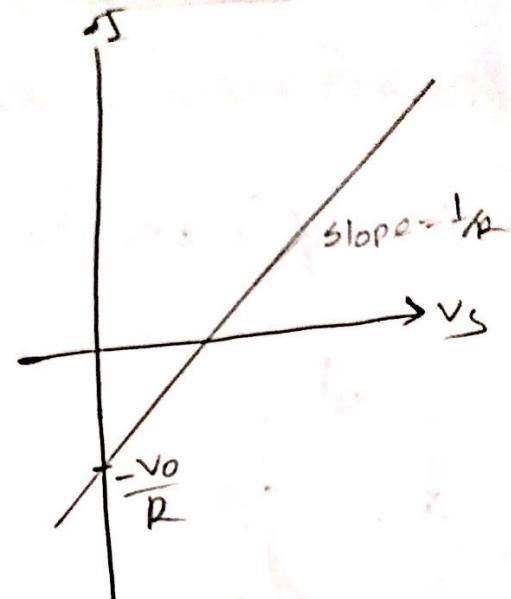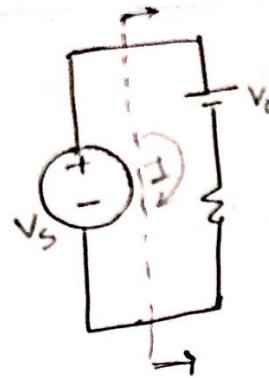


③ Current + resistor

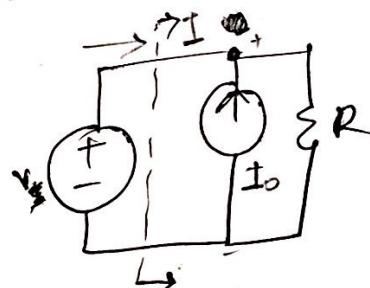

$$I + I_o = \frac{V}{R}$$
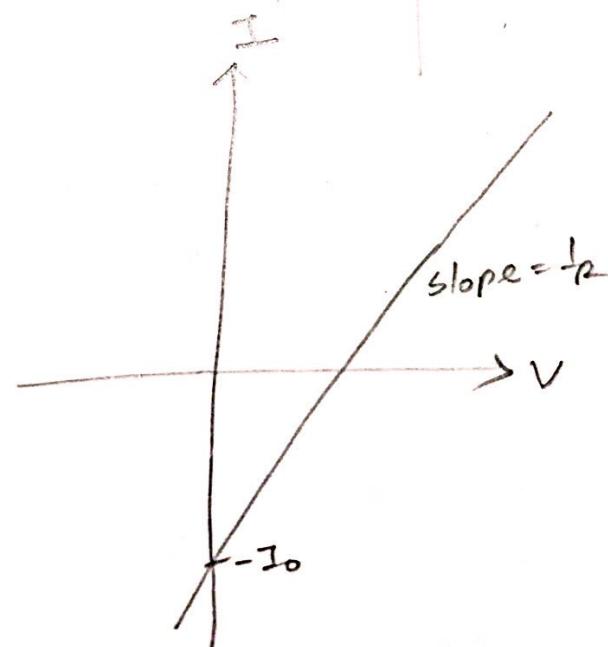
$$\Rightarrow I = \left(\frac{1}{R} \cdot V - I_o \right)$$




② Voltage source.

③ and ④ are same ~~at the top right~~

$$\left(I_o = \frac{V_o}{R} \right) \text{ or } V_o = I_o R$$


Slope = 0 \rightarrow Resistor(∞)

Slope = (-) ∞ Non-existent element.

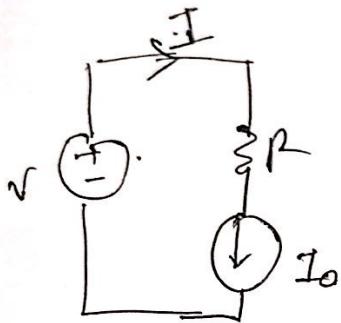


V	I
5V	I_o
6V	I_o

$$I = I_o$$

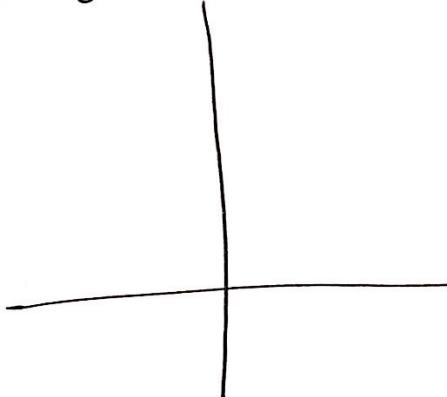

Open Loop

(1) comparators:

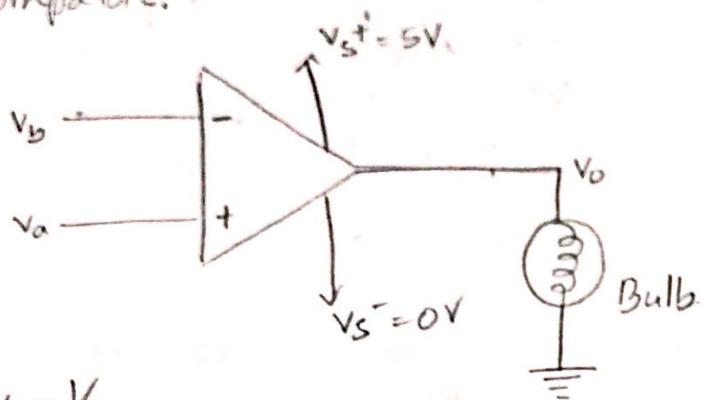

$$V_d = V_a - V_b$$

$V_d > 0 \Rightarrow V_a > V_b \rightarrow (V_S^+) \rightarrow V_o = 5V = \text{Bulb on}$


$V_d < 0 \Rightarrow V_a < V_b \rightarrow (V_S^-) \rightarrow V_o = 0V = \text{Bulb off}$

Open Loop





(2) No connection between output and input in physical configuration. (free floating)

$$V_o (-10 < V_I < 10)$$

~~Feedback~~ creating control system

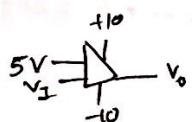

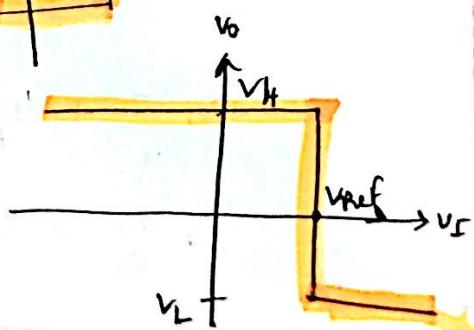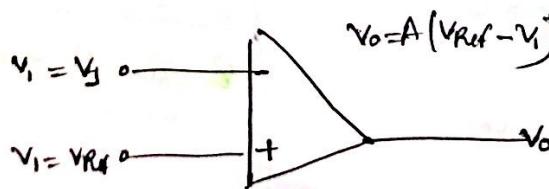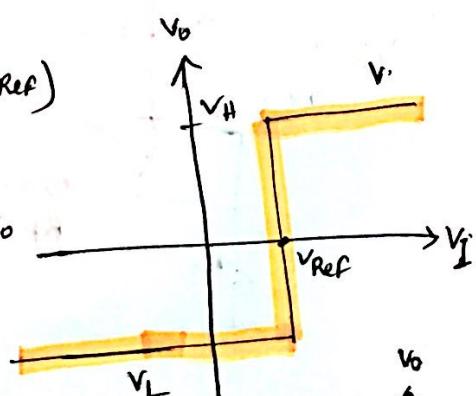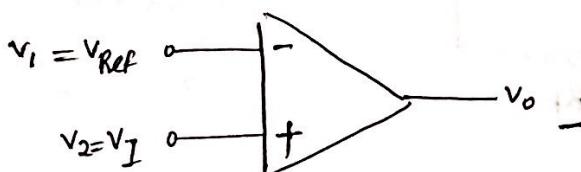
$$\begin{aligned} V_d &= V_2 - V_1 \\ &= V_I - 5 \\ &\Rightarrow -10 - 5 \Rightarrow -15 \\ &\Rightarrow -9 - 5 \Rightarrow -9 \\ &\Rightarrow 0 - 5 \Rightarrow -5 \\ &\Rightarrow 5 - 5 \Rightarrow 0 \\ &\Rightarrow 6 - 5 \Rightarrow 1 \\ &\Rightarrow 10 - 5 \Rightarrow 5 \end{aligned}$$



③

Negative feedback

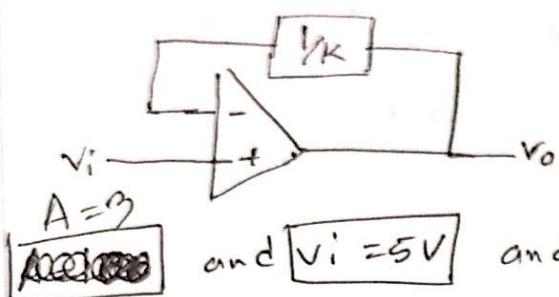

$k=10 \Rightarrow (V_o)$ etc. of output
is feedback to
 \rightarrow input.

if no feedback.

$$V_o = A V_i$$

$$= 15 \text{ V}$$

$$\begin{aligned} V_d & (+) \\ 9.2 & \\ V_{st} & \\ 2.5 & \times 10^3 \end{aligned}$$

$$V_o = 0 \text{ V} \quad \text{connect across } 2.5 \times 10^3$$

$$V_- = \frac{V_o}{10} = 0$$

$$\begin{aligned} V_d &= V_+ - V_- \\ &= 5 - 0 \\ &= 5 \end{aligned}$$

$$\begin{aligned} V_o &= A V_d \\ V_o &= 5 \times 3 \\ &= 15 \end{aligned}$$

Connection op-amp

$$V_o = 15 \text{ V}$$

$$V_- = \frac{15}{10} = 1.5 \text{ V}$$

$$\begin{aligned} V_d &= V_+ - V_- \\ &= 5 - 1.5 \\ &= 3.5 \end{aligned}$$

$$\begin{aligned} V_o &= 3.5 \times 3 \\ &= 10.5 \end{aligned}$$

$$V_o = 10.5$$

$$V_- = \frac{10.5}{10} = 1.05$$


$$\begin{aligned} V_d &= V_+ - V_- \\ &= 5 - 1.05 \\ &= 3.95 \end{aligned}$$

$$\begin{aligned} V_o &= 3.95 \times 3 \\ &= 11.85 \end{aligned}$$

$$V_- = \frac{11.85}{10} = 1.185$$


$$V_d = 5 - 1.185 = 3.815$$

$$V_o = 11.445$$

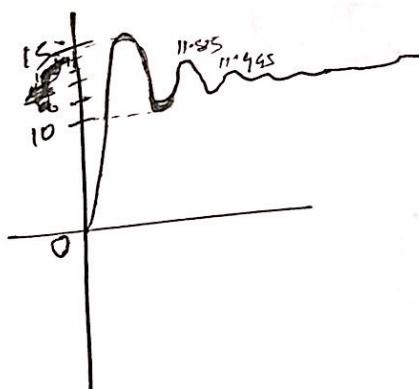


graph

Diode

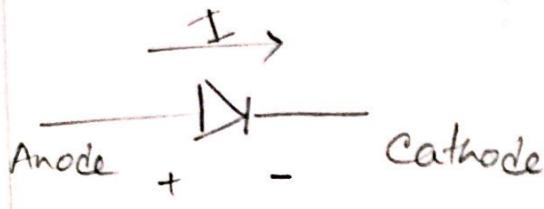


- D +
current flow 210 A

V-I characteristic of diode

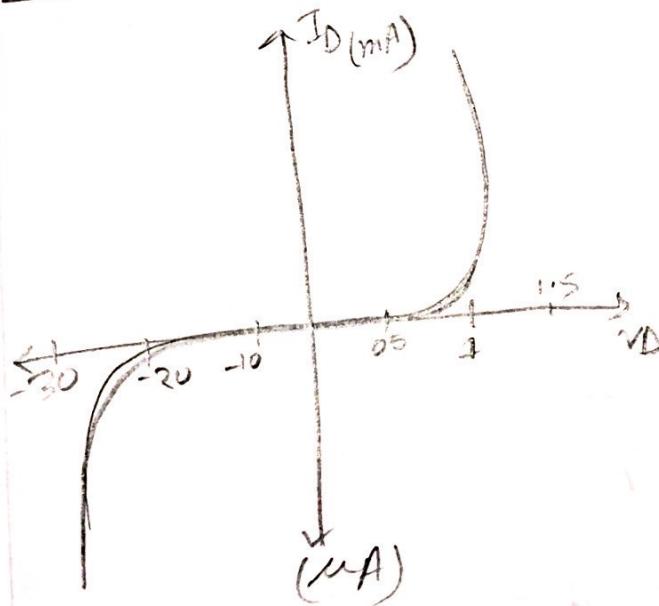


5V

V_D

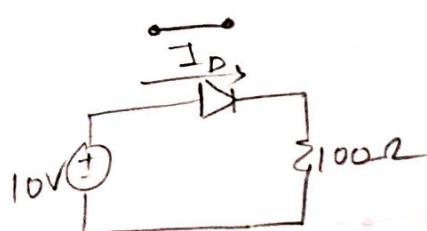


$$I_D = \frac{10}{100} A \\ = 0.1 A$$

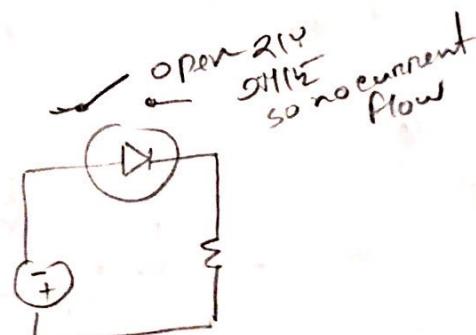


(6)

Buffer configuration:

(Non-inverting)

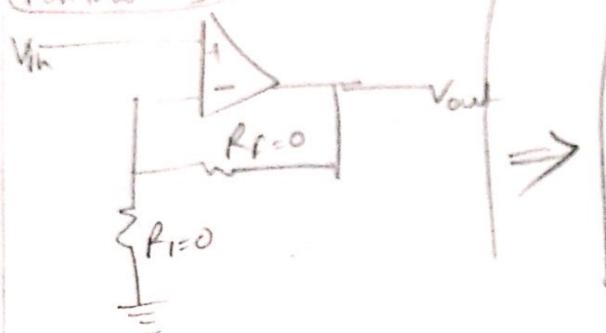

Buf

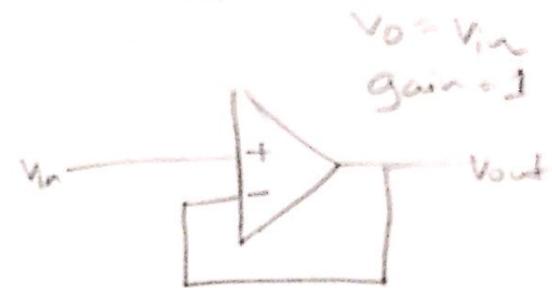

$$\text{gain} = \left(1 + \frac{R_f}{R_1}\right) = \left(1 + \frac{0}{\infty}\right) = 1$$

$$V_o = V_{in}$$

Design Problems.

$$\textcircled{1} \quad V_o = -4V_1 + \frac{V_2}{4}$$

$$\textcircled{1} \quad V_o = 3V_1 + 4V_2 + 0.5V_3$$

Non-inverting

$$1 + \frac{R_f}{R_1}$$


Inverting

$$-\frac{R_f}{R_1}$$


Adder.

$$-\sum \frac{R_f}{R_1} \cdot V_i$$



(1) ~~for 5A 5B~~,
for 5A 5B

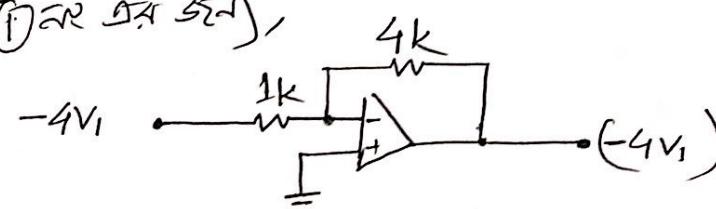


$$-(-k_1 V_2)$$

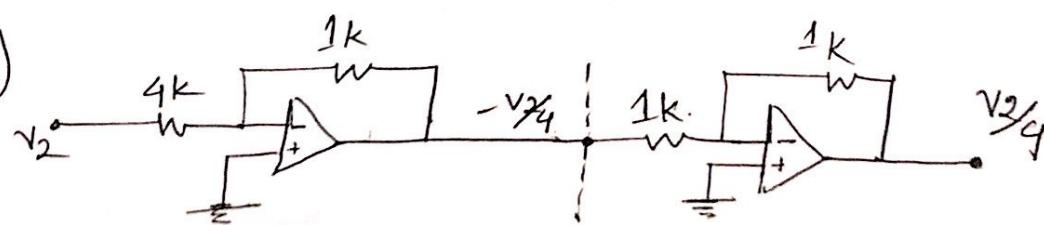


i 82.

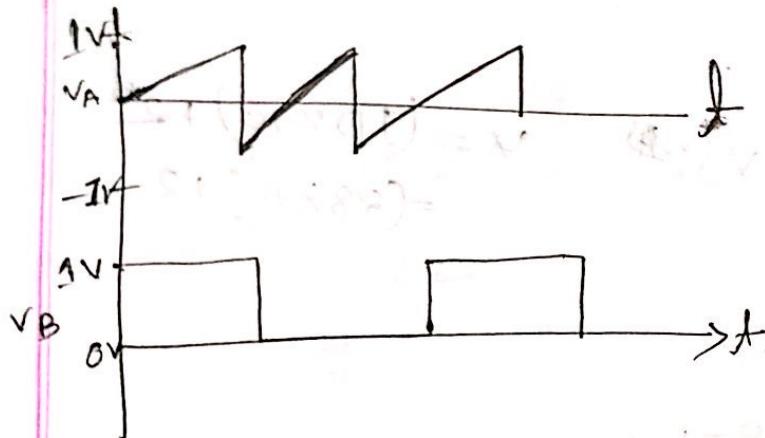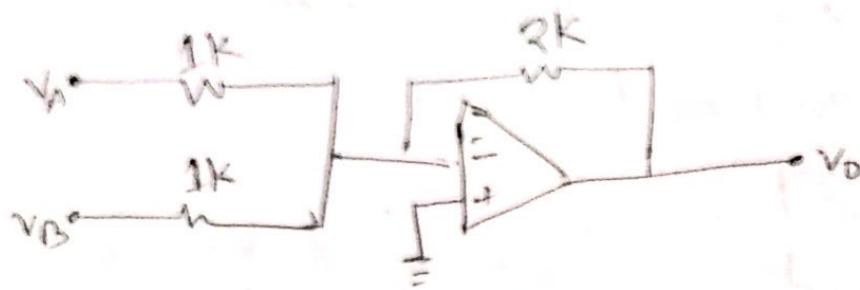
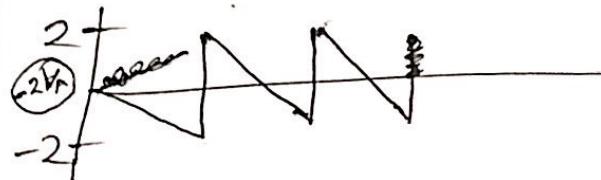
$$v_o = -\left(\frac{2}{1} v_A + \frac{2}{1} v_B\right) = -2v_A - 2v_B$$


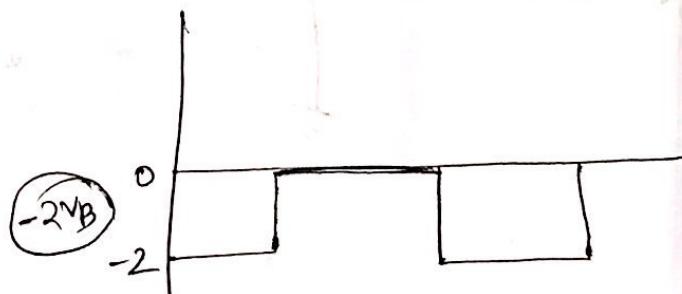
$$\begin{aligned} -2xv_A &= -2x1 \\ &= -2 \\ -2 & \\ 2xv_A &= 2x1 \\ &= +2 \end{aligned}$$




$g_2 k_2 / g_1 k_1$

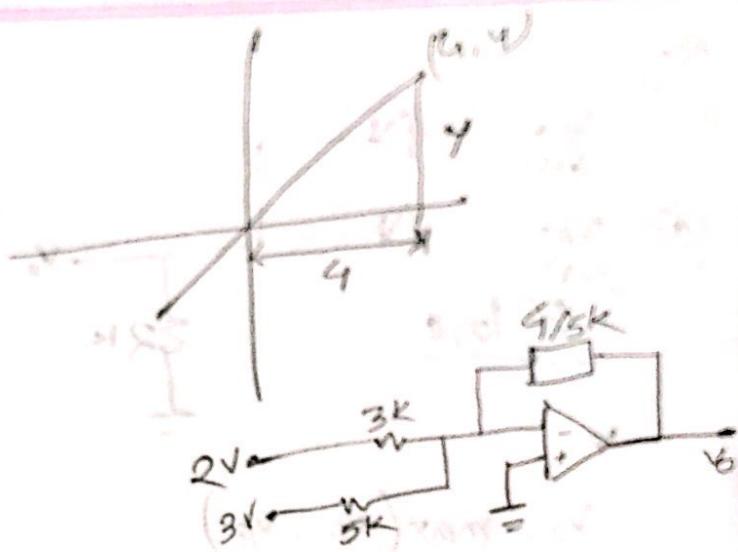
Q9. $n = \text{Resistance}$


$$R = \frac{g}{Y} \\ = \frac{1}{5} (\text{let})$$

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \\ = - \cancel{\frac{4000}{5 \times 3}} \left(\frac{4}{5 \times 3} \times 2 + \frac{4}{5 \times 5} \times 3 \right)$$





Q10:

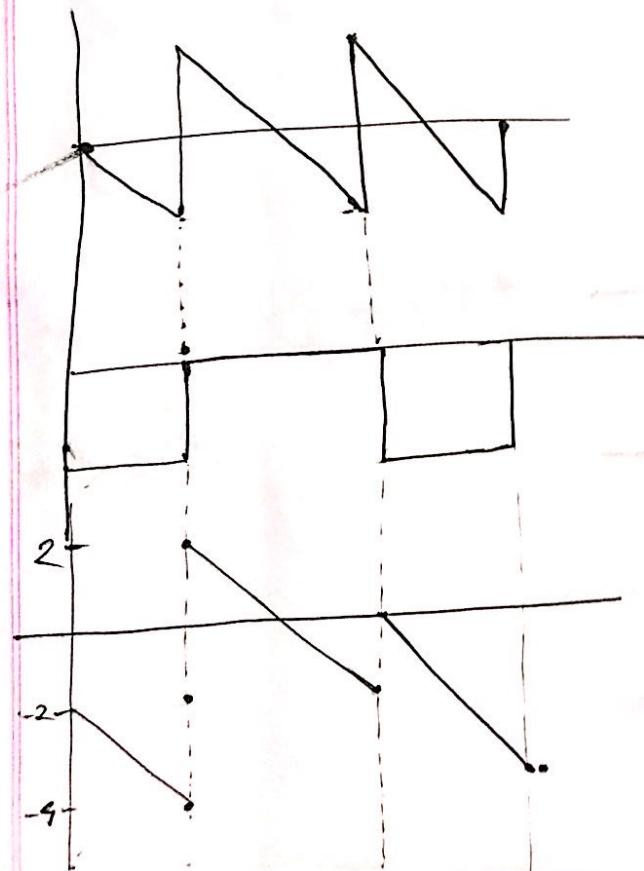

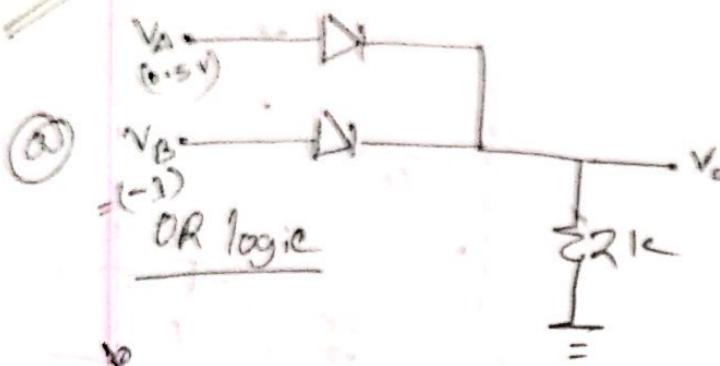


$$V_o = \max(V_A, V_B)$$

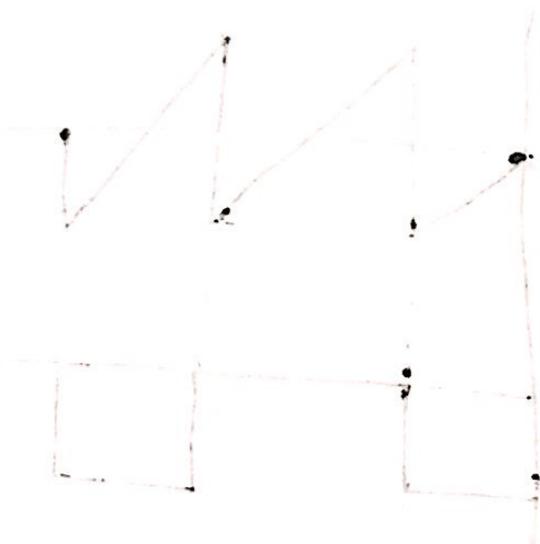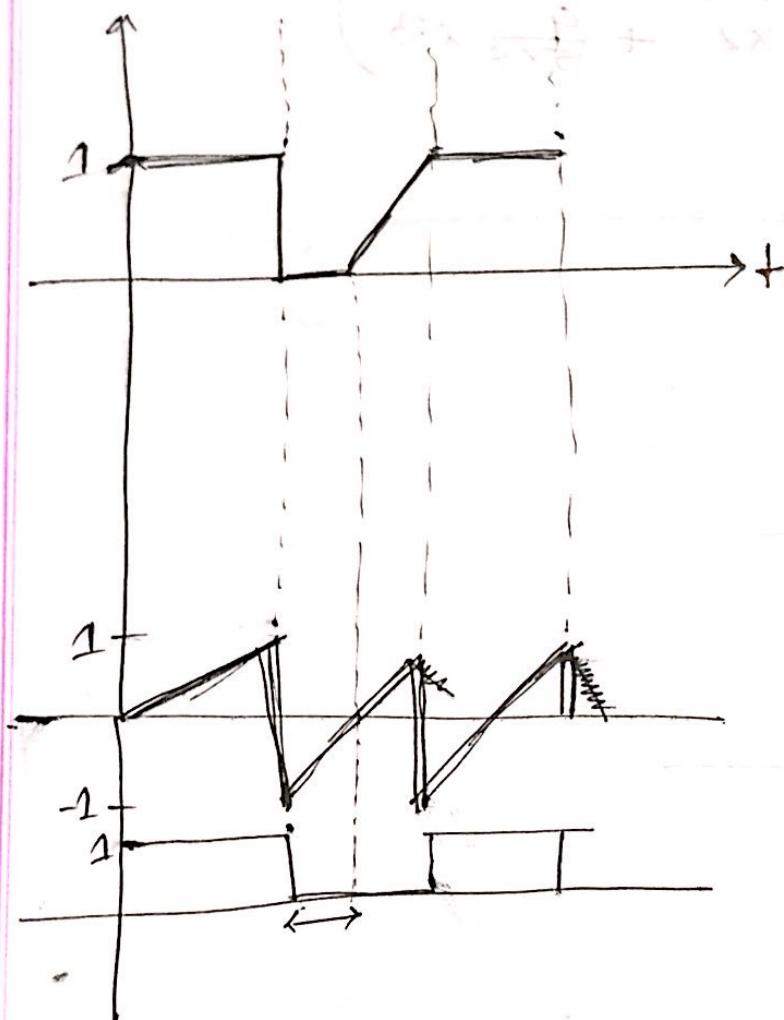for anti di 27a1w Diode = Ideal ($V_d > 0, V < 0$)




diode voltage with 1.32V Diode on 20⁻²

- one 2.5V var - linear circuit

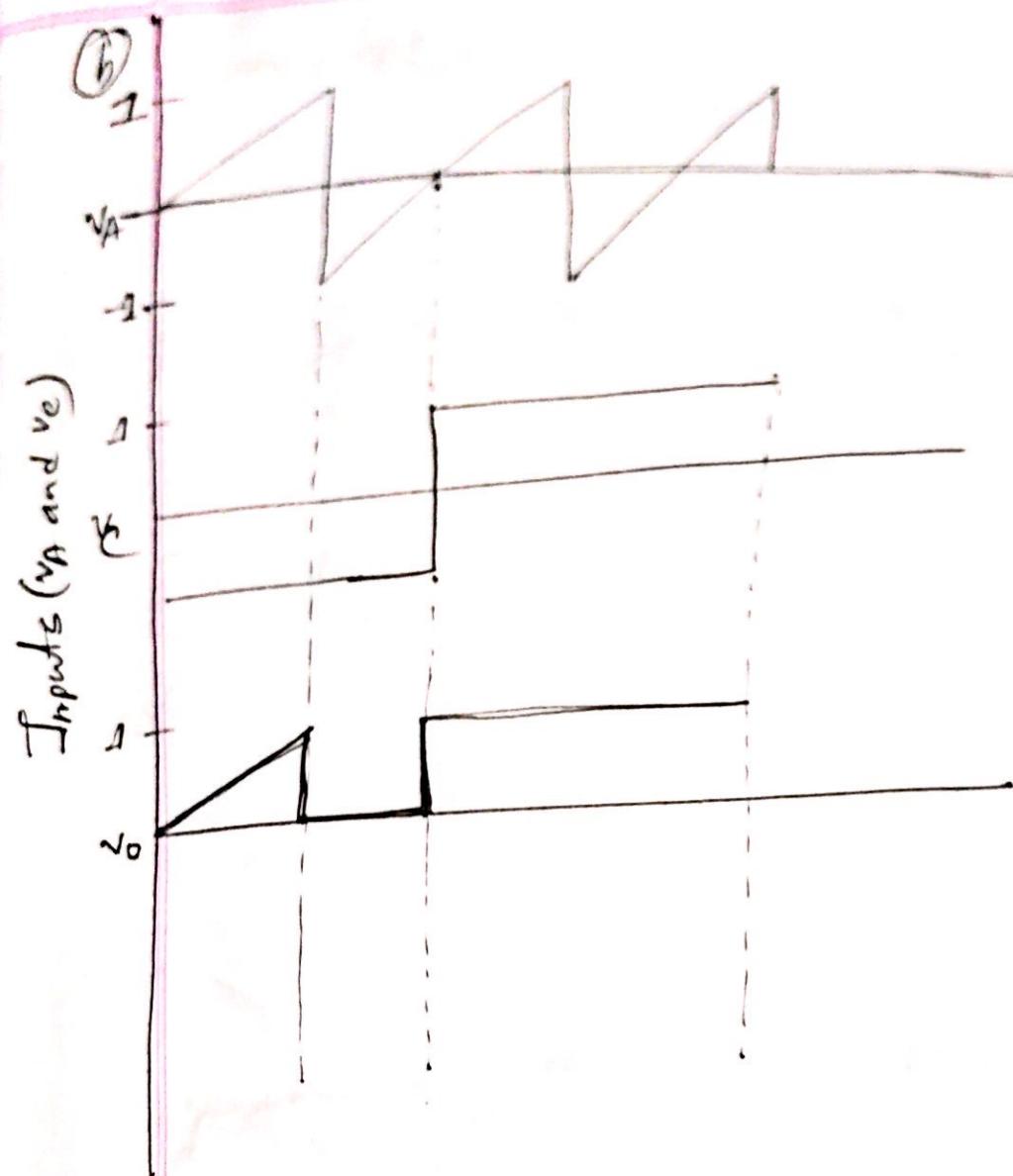

$$v_0 = \max\{v_A, v_C\}$$

$$\Rightarrow v_0 > 0$$

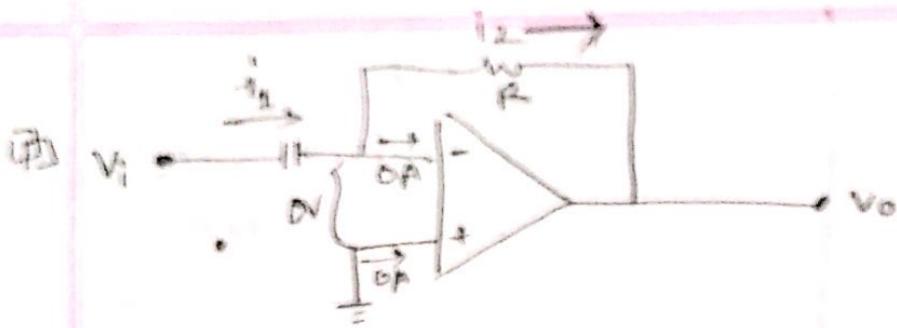


$$\text{At in} \Rightarrow \frac{(V_i - 0)}{R} = \frac{V_i}{R}$$

$$i_2 = C \cdot \frac{dV_i}{dt} = C \cdot \frac{d(V_o - V_i)}{dt} \\ = -C \cdot \frac{dV_o}{dt}$$

$$\because i_1 = i_2 \Rightarrow \frac{dV_o}{dt} = -\frac{V_o}{RC}$$
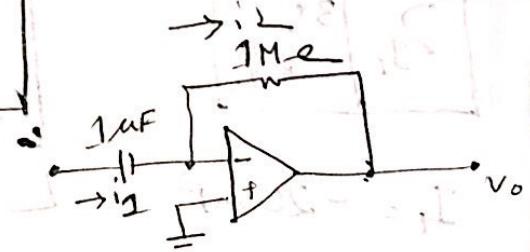
$$\Rightarrow V_o = -\frac{1}{RC} \int V_i dt$$



$$\text{b) } V_o = -RC \cdot \frac{dV_i}{dt}$$

$$\omega_R = 1 \text{ rad/s}$$

$$C = 1 \mu F$$

$$RC = 1 \text{ sec}$$

$$\frac{d}{dt} (0.25 \sin(2\omega t)) \\ = 0.25 \cos 2\omega t \times 2\omega$$

$$\omega = 5 \cos 2\omega t$$

$$V_o = (-1 \times 5 \cos(2\omega t)) \\ = -5 \cos(2\omega t)$$

$$\frac{i_1 = i_2}{i_2 = \frac{0 - (-5\cos 20t)}{1 \text{ M} \cdot \Omega}} = 5 \times 10^{-6} \cos 20t \text{ A}$$

$$= 5 \cos 20t \text{ mA}$$

B

integrate
diff
invert

add.
 $v_2 = v < \rightarrow v < \sqrt{v}$

$-v = v < \rightarrow v > \sqrt{v}$

$$V_{I_1} = -\frac{dy}{dt}$$

$$V_{I_2} = -\frac{5}{8} (V_{I_1}) = \frac{dy}{dt}$$

$$V_{I_3} = -\int y dt$$

$$f = -\frac{R_F}{R_1} V_{I_2} - \frac{R_F}{R_1} V_{I_3}$$

$R_F = 5$
 $R_1 = 5$


$$= -V_{I_2} - V_{I_3}$$

$$= -\frac{dy}{dt} + \int y dt$$

$y = 2 \sin 50t$
 $y = 5 \cos 32t - 7 \sin 3t$
at $t = 5 \text{ sec}$,
 $f = ?$

$y = 2 \sin 25t$
 $y = \sin 2t - \cos 3t$
at $t = 5 \text{ sec}$,
 $f = ?$

Q3 Buffer configuration (config 2.1)

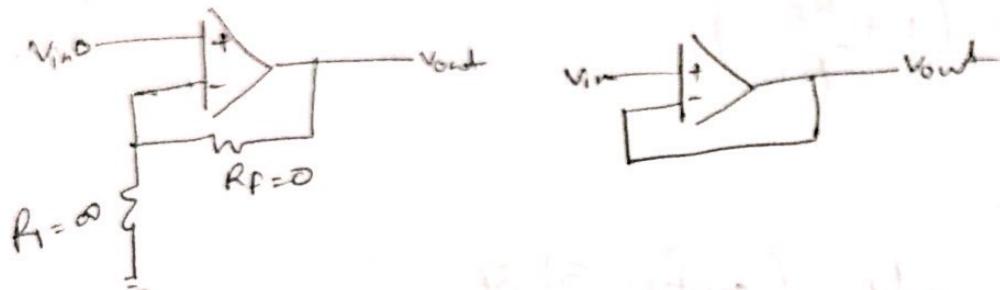

$$\text{gain} = 1 + \frac{R_f}{R_i} = \left(1 + \frac{0}{\infty}\right) = 1$$

$$V_o = V_{in}$$

Q4 Design problems. (from Q - 24 MARCH)

$$\textcircled{I} V_o = -4V_1 + V_2/4$$

$$\textcircled{II} V_o = -3V_1 + 4V_2 + 0.5V_3$$

Non-inverting

$$1 + \frac{R_f}{R_i}$$

Inverting


$$-R_f/R_i$$

Adder

$$-\sum \frac{R_f}{R_i} \cdot v_i$$


$$\textcircled{I} V_o = -4V_1 + V_2/4$$


$$-4V_1$$

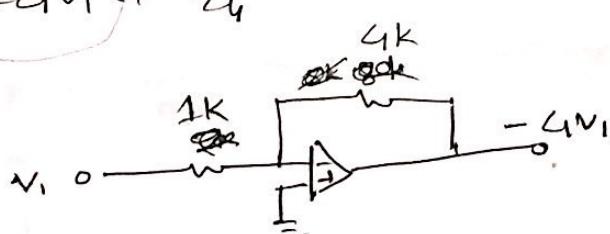

$$-(0.25V_2)$$

$$V_2$$

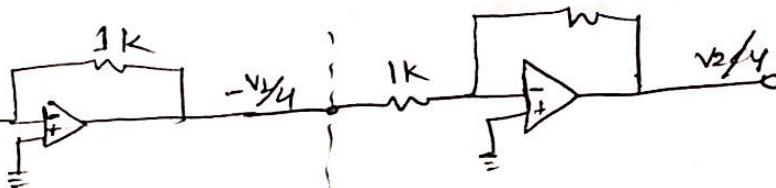

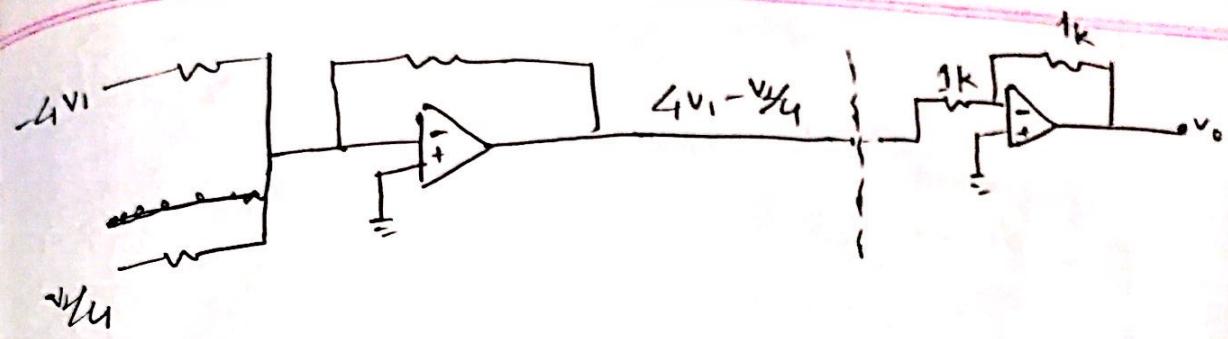

$$\begin{aligned}
 \textcircled{1} \quad v_0 &= (-3v_1 + 4v_2 + 0.5v_3) \\
 &= -(3v_1 - 4v_2 - 0.5v_3)
 \end{aligned}$$

